

9. Coupling

Two tuned circuits handing energy back and forth


Lesson 9 · about 75 minutes · everyone builds; battery power only

What you need

- Two identical pendulums — same length, same weight
- A horizontal string or dowel to hang them from
- Two identical LC tanks from Lesson 8
- Signal generator and oscilloscope, or the multimeter method
- A ruler, to set and measure coil spacing

Predict first

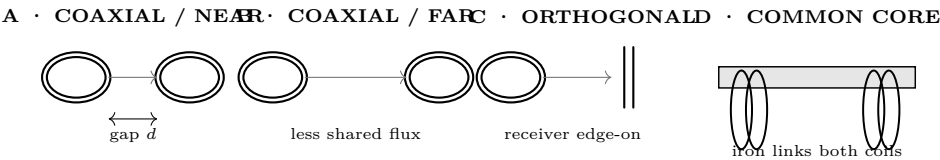Two identical pendulums hang from the same slack string. You start one swinging and hold the other still, then let go. What happens to each over the next minute? Draw both, one under the other, against time.



Do it — establish the mechanical model

- Hang two identical pendulums from a common horizontal string with some slack in it. Start one; leave the other at rest.
- Every five seconds, record both amplitudes. Continue through one complete transfer out and back. Do not merely write “it moved.”
- Tighten the support string and repeat. Then slacken it and repeat. Graph the two amplitudes against time. Which setting changes transfer time?
- Shorten one pendulum by 10%, restore the middle string tension, and repeat. This separates frequency mismatch from coupling strength.

Pendulum state record						
State	0 s	5 s	10 s	15 s	20 s	transfer time
Matched / slack						
Matched / tight						
Detuned / middle						

Then the coils — geometry before resonance

- Disconnect both capacitors. Pulse the transmitter coil from the two AA cells through a pushbutton. Connect only the receiver coil to the meter. Tape the leads so they cannot masquerade as a geometry effect.
- At every state, make five equal presses and record the median absolute receiver pulse. Confirm that the break pulse reverses sign. Stop for warmth.
- Keep both coil axes coincident and repeat at $d = 0, 1, 2, 4, 8$ cm.

- Return to $d = 2$ cm. Rotate the receiver about its center through $0^\circ, 30^\circ, 60^\circ, 90^\circ$.
- Repeat the full distance series with a removable iron core linking both coils. Remove it and recover the original baseline before proceeding.

Repeated distance $\times$ core matrix				
d (cm)	air: median $ V $	core: median $ V $	core/air	spread, anomaly, or control note
0				
1				
2				
4				
8				

Repeated orientation matrix at $d = 2$ cm				
θ	median $ V $	fraction of 0°	projected-area prediction	pulse sign
0°		1.00	maximum	
30°				
60°				
90°			near minimum	

Restore the two tuned tanks

- Reconnect the identical capacitors and set the coils coaxial at $d = 4$ cm. Sweep across the Lesson 8 resonance in equal frequency steps. Record transmitter and receiver amplitudes.
- Repeat at $d = 2$ cm and $d = 1$ cm without changing sweep range or drive. Look for one peak becoming two; do not assume it.
- Change only the receiver capacitor. Repeat at $d = 2$ cm. Then restore the capacitor and verify the original curve returns.

Frequency-sweep matrix						
State	f_1	f_2	f_3	f_4	f_5	peak(s)
$d = 4$ cm / matched						
$d = 2$ cm / matched						
$d = 1$ cm / matched						
$d = 2$ cm / detuned						


What it means

Coupling coefficient	Written k , from 0 (no shared field) to 1 (all of it shared). Here, distance, orientation, and core all change k .
Why loose is better here	Energy takes many cycles to cross a loosely coupled pair, and during those cycles the secondary's voltage builds and builds. Couple them tightly and the transfer is fast but the secondary never gets the chance to ring up. Tight coupling also puts so much voltage across the secondary's own turns that it arcs internally and destroys itself.
Both must be tuned the same	This is what the pendulum experiment proves. Coupling with mismatched frequencies transfers almost nothing.
Energy goes both ways	The pendulums traded back and forth, and so do the coils. In a real coil we want the transfer stopped at the moment the secondary is fullest — which is exactly what the spark gap does in Lesson 10, by quenching.
This is why it is not a transformer	A transformer trades voltage for current by turns ratio alone. A Tesla coil does that <i>and</i> accumulates energy over many cycles of a shared resonance. That second mechanism is where most of the voltage comes from.

Questions that make the graphs earn their ink	
1. Which trial is the baseline?	9. Which result isolates lead length?
2. Did all five pulses agree?	10. Why compare pulse magnitude, not held voltage?
3. What changed when d doubled?	11. Why does break polarity reverse?
4. Is the distance relation linear?	12. Which changes k , and which changes tuning?
5. Why keep the axes coincident?	13. When did one resonance become two?
6. Was 90° exactly zero?	14. Did detuning resemble the short pendulum?
7. What stray paths explain a nonzero minimum?	15. What result would falsify your claim?
8. Did the core give one constant multiplier?	16. Where does meter resolution limit it?

Graph, diagnose, prove

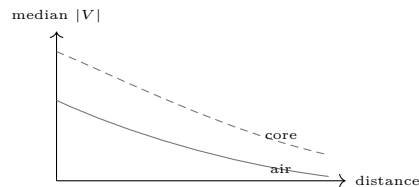Three required graphs. Plot air and core pulse magnitude against distance on shared axes. Plot normalized pulse against angle. Plot receiver amplitude against frequency for every matched spacing and the detuned state. Show measured points; connect them only as guides. Mark readings below resolution and label both split peaks if they exist.



Fault isolation	Symptom	Discriminating check
	No pulse	Verify range, receiver continuity, then transmitter current.
	Only lead motion works	Tape leads; press without touching coils.
	Trials scatter	One operator; inspect button; use the median.
	90° stays large	Remove metal; shrink lead loops; recenter.
	No resonant peak	Verify each tank alone before coupling them.
	Core seems weaker	Restore air baseline; ensure core links both coils.

BLIND FINAL PROOF
A partner hides two receiver states behind a sheet, choosing from coaxial/near, coaxial/far, orthogonal, common-core, or detuned. Take five pulse readings and, where needed, a short frequency sweep. Identify both states and justify them from all three graphs. Swap roles. The proof passes only when both partners identify both states, recover the starting baseline within its measured spread, and observe opposite make/break pulse signs. Diagnose before repeating; never erase a failed trial.

The whole machine, in one sentence you can now parse

The transformer charges the capacitor; the gap dumps it into the primary tank, which rings at f_0 ; the secondary is tuned to the same f_0 and loosely coupled, so over many cycles it takes that energy and rings up to a voltage far higher than the transformer alone could make; and the gap quenches at the right moment so the energy does not slosh back. Lessons 6, 7, 8 and 9 are those four clauses.

This lesson is low voltage. Everything here runs from batteries or a small plug-in supply and cannot hurt you. That changes at Lesson 10. Build the habits now — one hand, discharge before touching, check before you power up — while the stakes are nothing, so that they are automatic when the stakes are real.

Telos. Electricity & Magnetism — 9. Coupling. Revised 2026-07-25. Project-created text and diagrams are licensed CC BY 4.0. Incorporated public-domain artwork remains public domain and is credited on the plate it appears with. See `LICENSE` and `CREDITS.md` in the source. Nothing here is professional advice; verify current regulations and follow the stated safety procedure.